

# LM3492 Evaluation Board Reference Design

National Semiconductor  
Application Note 2056  
L.K. Wong  
September 21, 2010



## Introduction

The LM3492 integrates a boost converter and a two-channel current regulator to implement a high efficient and cost effective LED driver for driving two individually dimmable LED strings with a maximum power of 15W and an output voltage of up to 65V. The boost converter employs a proprietary Projected-On-Time control method to give a fast transient response with no compensation required, and a nearly constant switching frequency programmable from 200 kHz to 1 MHz. The application circuit is stable with ceramic capacitors and produces no audible noise on dimming. The programmable peak current limit and soft-start features reduce current surges at startup, and an integrated 190 mΩ, 3.9A N-Channel MOSFET switch minimizes the solution size. The fast slew rate current regulator allows high frequency and narrow pulse width dimming signals to achieve a very high contrast ratio of 1000:1 at a dimming frequency of more than 3 kHz. The LED current is programmable from 50 mA to 200 mA by a single resistor.

To maximize the efficiency, Dynamic Headroom Control (DHC) automatically adjusts the output voltage to a minimum.

DHC also facilitates a single BOM for different number of LED in a string, which is required for backlight panels of different size, thereby reducing overall development time and cost. The LM3492 comes with a versatile COMM pin which serves as a bi-directional I/O pin interfacing with an external MCU for the following functions: power-good, over-temperature, IOUT over- and under-voltage indications, switching frequency tuning, and channel 1 disabling. Other supervisory functions of the LM3492 include precise enable, VCC under-voltage lock-out, current regulator Over-Power protection, and thermal shutdown protection. The LM3492 is available in the thermally enhanced eTSSOP-20 package.

This application note details the design of a LM3492 evaluation board which drives 2 LED strings, each of which consists of 10 LEDs running at 150 mA and the forward voltage of each LED is typically 3.8V. The input voltage is from 9V to 16V. The evaluation board schematic, PCB layout, Bill of Materials, and circuit design descriptions are shown. Typical performance and operating waveforms are also provided for reference.

## Evaluation Board Schematic and PCB Layout

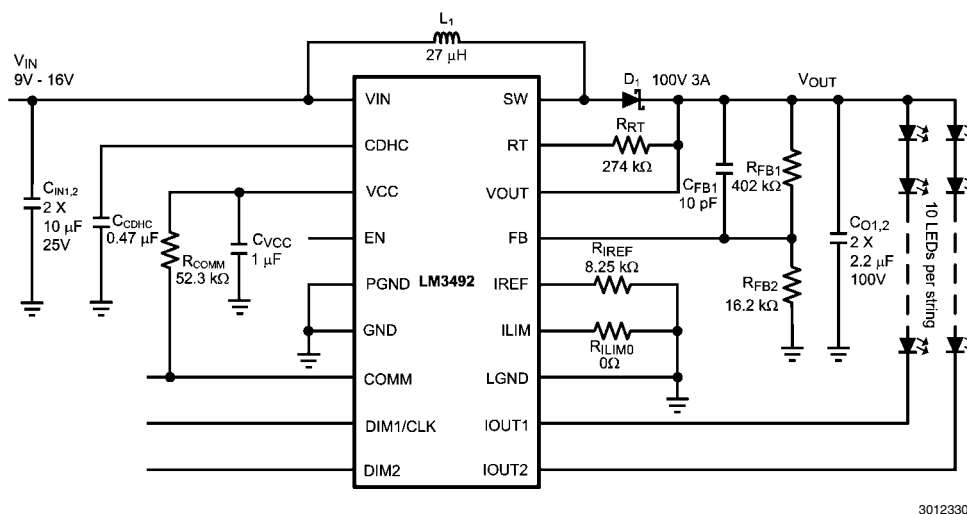


FIGURE 1. LM3492 Evaluation Board Schematic

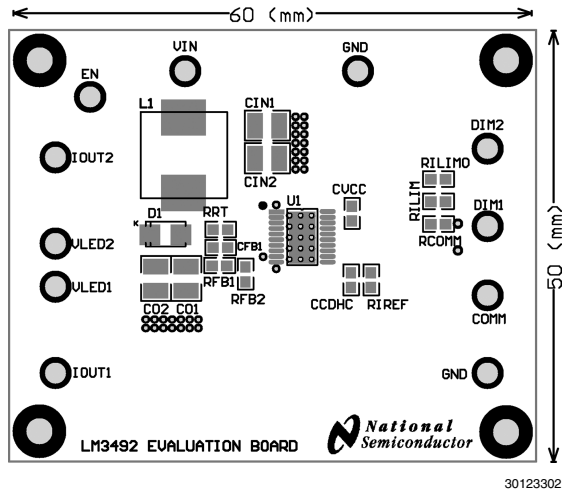


FIGURE 2. LM3492 Evaluation Board Top Overlay

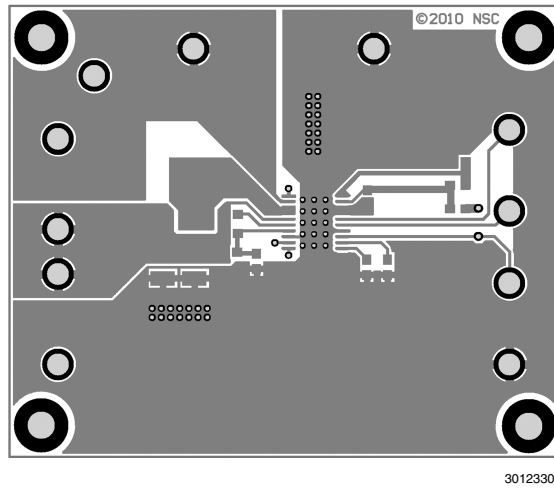


FIGURE 3. LM3492 Evaluation Board Top View

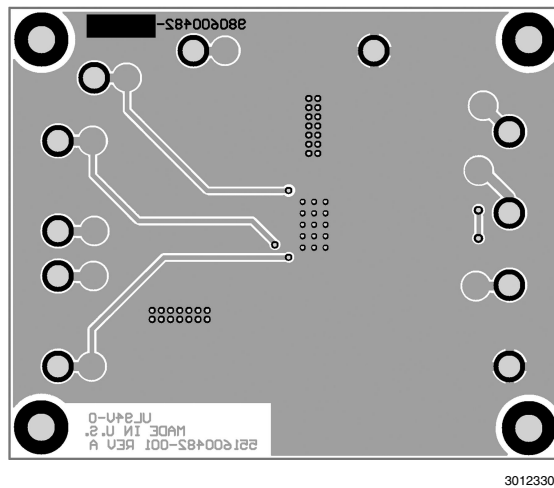


FIGURE 4. LM3492 Evaluation Board Bottom View

## Evaluation Board Quick Setup Procedures

Step	Description	Notes
1	Connect a power supply to VIN and PGND terminals	V <sub>IN</sub> range: 9V to 16V
2	Connect 2 LED strings: from VLED1 to IOUT1 terminals, and VLED2 to IOUT2 terminals	Each LED string consists of 10 LEDs with a forward voltage of 3.8V per LED at 150 mA
3	The EN terminal should be left open for normal operation. Ground this terminal to shutdown	
4	Connect DIM1 and DIM2 terminals to a voltage > 2V, apply V <sub>IN</sub> = 12V	Nominal LED current is 150 mA per channel
5	Ground the EN terminal to check the shutdown function	

## Evaluation Board Performance Characteristic

Description	Symbol	Condition	Min	Typ	Max	Unit
Input Voltage	V <sub>IN</sub>		9	12	16	V
Rail Voltage	V <sub>OUT</sub>			39		V
LED Current	I <sub>LED</sub>			150		mA
LED Current Regulation	ΔI <sub>LED</sub>	ALL V <sub>IN</sub> conditions	-3		+3	%
Efficiency		V <sub>IN</sub> = 9V		85.7		%
		V <sub>IN</sub> = 12V		88.2		%
		V <sub>IN</sub> = 16V		89.1		%

## Design Procedure

The following procedures detail the design of the LM3492 evaluation board driving 2 LED strings consists of 10 LEDs per string. The forward voltage of each LED is 3.8V, and the LED current is 150 mA. The input voltage is ranged from 9V to 16V. The switching frequency  $f_{SW}$  is designed to be 500 kHz.

## Design Parameters:

V<sub>IN</sub> = 9V to 16V, typical 12V

I<sub>LED</sub> = 150 mA

## Step 1: Calculate the output voltage feedback circuit

The nominal voltage of the LED string with 10 LEDs is 38V, and the minimum voltage of the IOUTn pin (n = 1, 2) is 0.75V for an I<sub>LED</sub> of 150 mA. Hence, V<sub>OUT(NOM)</sub> is 38.75V. Since the dynamic range of V<sub>FB</sub> under DHC is from 1.05V to 2V, the nominal voltage on the FB pin V<sub>FB(NOM)</sub> is designed to be around 1.5V. Hence, V<sub>OUT(MAX)</sub> is designed to be 65V. Since

$$V_{OUT(MAX)} = 2.5V (1 + R_{FB1}/R_{FB2}) \quad (1)$$

By designing R<sub>FB2</sub> to be 16.2 kΩ, R<sub>FB1</sub> is calculated to be 405 kΩ, and a standard resistor value of 402 kΩ is selected. C<sub>FB1</sub> is selected to be 10 pF as recommended.

## Step 2: Determine the inductance

The main parameter affected by the inductor is the peak to peak inductor current ripple (I<sub>LR</sub>). To maintain a continuous conduction mode (CCM) operation, the average inductor current I<sub>L1</sub> should be larger than half of I<sub>LR</sub>.

For a boost converter, I<sub>L1</sub> equals to the input current I<sub>IN</sub>. The minimum I<sub>IN</sub> occurs when V<sub>IN</sub> is maximum, which is 16V in this example, and only 1 LED string is turned on (the 2 LED strings are individually dimmable). Hence,

$$I_{IN(MIN)} = (V_{OUT(NOM)} \times I_{LED}) / V_{IN(MAX)} \quad (2)$$

Also

$$t_{on} = (1 - V_{IN}/V_{OUT}) / f_{SW} \quad (3)$$

To ensure a CCM operation,

$$L_1 = (V_{IN(MAX)} \times t_{on}) / 2I_{IN(MIN)} \quad (4)$$

It can be calculated that I<sub>IN(MIN)</sub>, t<sub>on</sub>, and L<sub>1</sub> are 0.363A, 1.17 μs, and 25.8 μH. On the other hand, I<sub>IN</sub> is maximum when V<sub>IN</sub> is minimum, which is 9V in this example, and 2 LED strings are turned on. Hence I<sub>IN(MAX)</sub> is 1.29A. From (3), t<sub>on</sub> is 1.54 μs when V<sub>IN</sub> is 9V. Then I<sub>LR</sub> is

$$I_{LR} = (V_{IN} \times t_{on}) / L_1 \quad (5)$$

From (5), I<sub>LR</sub> is 0.53A. The steady state peak inductor current I<sub>L1(PEAK)</sub> is

$$I_{L1(PEAK)} = I_{L1} + I_{LR} / 2 \quad (6)$$

As a result, I<sub>L1(PEAK)</sub> is 1.56A. A standard value of 27 μH is selected for L<sub>1</sub>, and the saturation current of L<sub>1</sub> should be larger than 1.56A.

## Step 3: Determine the diode

The selection of the boost diode D<sub>1</sub> depends on two factors. The first factor is the reverse voltage, which equals to V<sub>OUT</sub> in a boost converter. The second factor is the peak diode current at the steady state, which equals to the peak inductor current as shown in (6). In this example, a 100V 3A schottky diode is selected.

## Step 4: Determine the value of other components

**C<sub>IN</sub> and C<sub>OUT</sub>:** The function of the input capacitor C<sub>IN</sub> and the output capacitor C<sub>OUT</sub> is to reduce the input and output voltage ripples. Experimentation is usually necessary to determine their value. The rated DC voltage of capacitors used should be higher than the maximum DC voltage applied.

Owing to the concern of product lifetime, ceramic capacitors are recommended. But ceramic capacitors with high rated DC voltage and high capacitance are rare in general. Multiple capacitors connecting in parallel can be used for C<sub>IN</sub> and C<sub>OUT</sub>. In this example, two 10 μF 25V ceramic capacitor are used for C<sub>IN</sub>, and two 2.2 μF 100V ceramic capacitor are used for C<sub>OUT</sub>.

**C<sub>VCC</sub>:** The capacitor on the VCC pin provides noise filtering and stabilizes the LDO regulator. It also prevents false trig-

gering of the VCC UVLO.  $C_{VCC}$  is recommended to be a 1  $\mu\text{F}$  good quality and low ESR ceramic capacitor.

**$C_{CDHC}$ :** The capacitor at the CDHC pin mainly determines the soft-start time  $t_{SS}$ , i.e. the time for the output voltage to reach its maximum.  $t_{SS}$  is determined from the following equation:

$$t_{SS} = \frac{C_{CDHC} \times 2.25V}{120 \mu\text{A}} \quad (7)$$

In this example,  $C_{CDHC}$  is recommended to be a 0.47  $\mu\text{F}$  good quality and low ESR ceramic capacitor.

**$R_{RT}$  and  $R_{IREF}$ :** The resistors  $R_{RT}$  and  $R_{IREF}$  set the switching frequency  $f_{SW}$  of the boost converter and the LED current  $I_{LED}$  respectively. From the LM3492 datasheet,  $R_{RT}$  is selected to be 274  $\text{k}\Omega$  if  $f_{SW}$  is 500 kHz (Figure 1 of the datasheet), and  $R_{IREF}$  is selected to be 8.25  $\text{k}\Omega$  if  $I_{LED}$  is 150 mA (Figure 4 of the datasheet).

**$R_{COMM}$ :** Since the COMM pin is open drain, a resistor  $R_{COMM}$  of 52.3  $\text{k}\Omega$  is used to connect the VCC and COMM pins to implement a pull-up function.

## PC Board Layout

The layout of the printed circuit board is critical to optimize the performance of the LM3492 application circuit. In general,

external components should be placed as close to the LM3492 and each other as possible in order to make copper traces short and direct. In particular, components of the boost converter  $C_{IN}$ ,  $L_1$ ,  $D_1$ ,  $C_{OUT}$ , and the LM3492 should be closed. Also, the output feedback capacitor  $C_{FB1}$  should be closed to the output capacitor  $C_{OUT}$ . The ground plane connecting the GND, PGND, and LGND pins and the exposed pad of the LM3492 and the ground connection of the  $C_{IN}$  and  $C_{OUT}$  should be placed on the same copper layer.

Good heat dissipation helps optimize the performance of the LM3492. The ground plane should be used to connect the exposed pad of the LM3492, which is internally connected to the LM3492 die substrate. The area of the ground plane should be extended as much as possible on the same copper layer around the LM3492. Using numerous vias beneath the exposed pad to dissipate heat of the LM3492 to another copper layer is also a good practice.

## Bill of Materials


Item	Part Number	Mfg name	Part Description	Qty	Ref Designator(s)	Size
1	GRM31CR61E106KA12L	muRata	Cap 10 $\mu$ F 25V X5R	2	C <sub>IN1</sub> , C <sub>IN2</sub>	1206
2	GRM188R71C474KA88D	muRata	0603/X7R/0.47 $\mu$ F/16V	1	C <sub>CDHC</sub>	0603
3	GRM1885C2A100RA01D	muRata	0603/COG/10 pF/100V	1	C <sub>FB1</sub>	0603
4	GRM188R71C105KA12D	muRata	0603/X7R/1 $\mu$ F/16V	1	C <sub>VCC</sub>	0603
5	GRM32ER72A225KA35L	muRata	Cap 2.2 $\mu$ F 100V X7R	2	C <sub>O1</sub> , C <sub>O2</sub>	1210
6	CRCW060352K3FKEA	Vishay	Resistor Chip 52.3 k $\Omega$ 1%	1	R <sub>COMM</sub>	0603
7	CRCW0603274KFKEA	Vishay	Resistor Chip 274 k $\Omega$ 1%	1	R <sub>RT</sub>	0603
8	CRCW0603402KFKEA	Vishay	Resistor Chip 402 k $\Omega$ 1%	1	R <sub>FB1</sub>	0603
9	CRCW060316K2FKEA	Vishay	Resistor Chip 16.2 k $\Omega$ 1%	1	R <sub>FB2</sub>	0603
10	CRCW06038K25FKEA	Vishay	Resistor Chip 8.25 k $\Omega$ 1%	1	R <sub>IREF</sub>	0603
11	CRCW06030000Z0EA	Vishay	Resistor Chip 0 $\Omega$ 1%	1	R <sub>ILIM0</sub>	0603
12	CDRH10D68/ANP-270MC	Sumida	Inductor 27 $\mu$ H 1.9A	1	L <sub>1</sub>	10×10×6.8
13	SK310A-TP	Micro Commercial	Schottky 100V 3A	1	D <sub>1</sub>	SMA
14	1502-2k-ND	KEYSTONE	Terminal DBL Turret 0.109"L Brass	11	VIN, GND, PGND, VLED1, VLED2, IOUT1, IOUT2, DIM1, DIM2, COMM, EN	
15	LM3492EVAL	NSC	LM3492 demo board	1	PCB	
16	LM3492MH	NSC	IC LM3492	1	U1	eTSSOP-20

## Typical Performance and Waveforms

All curves and waveforms taken at  $V_{IN} = 12V$  with the evaluation board and  $T_A = 25^\circ C$  unless otherwise specified.


All curves and waveforms taken at  $V_{IN} = 12V$  with the evaluation board and  $T_A = 25^\circ C$  unless otherwise specified.

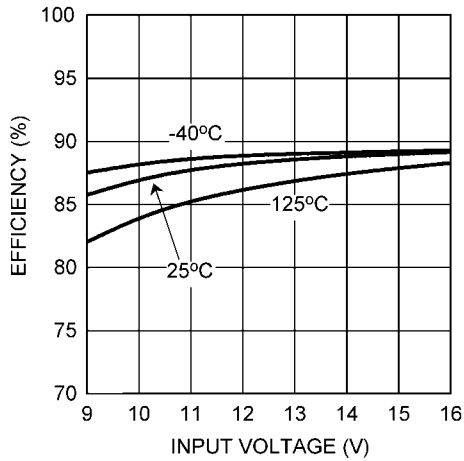**Efficiency vs Input Voltage**  
( $I_{LED} = 150\text{ mA}$ )




30123306

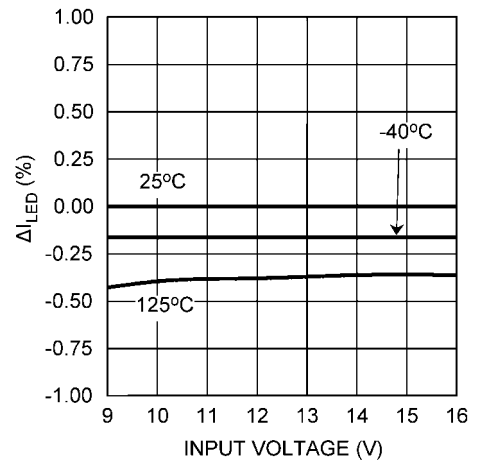**$I_{LED}$  Regulation vs Input Voltage**  
( $I_{LED} = 150\text{ mA}$ )




30123307

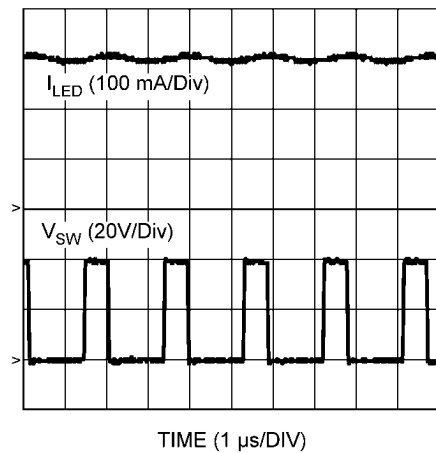**Steady State Operation**  
( $V_{IN} = 12V$ ,  $I_{LED} = 150\text{ mA}$ )




30123308

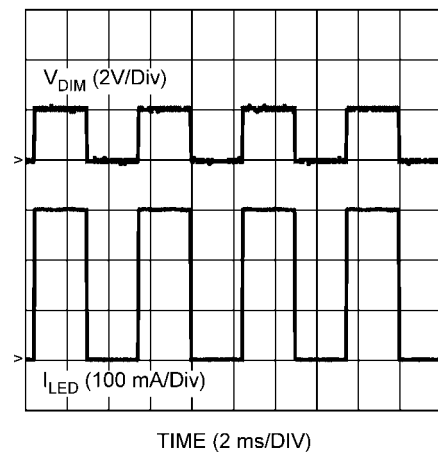**LED 50% Dimming**  
( $V_{IN} = 12V$ ,  $I_{LED} = 150\text{ mA}$ )




30123309

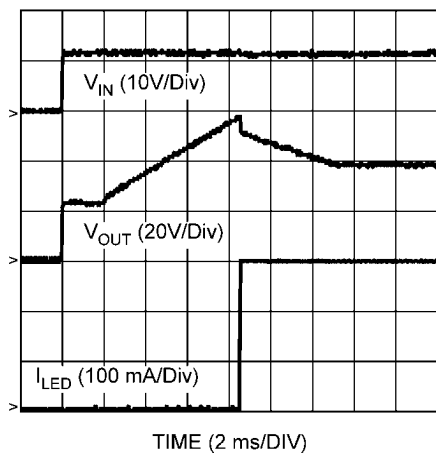**Power Up**  
( $V_{IN} = 12V$ ,  $I_{LED} = 150\text{ mA}$ )



30123310

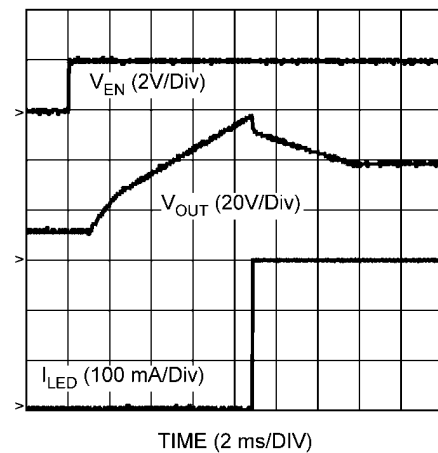**Enable Transient**  
( $V_{IN} = 12V$ ,  $I_{LED} = 150\text{ mA}$ )



30123311



## Notes

For more National Semiconductor product information and proven design tools, visit the following Web sites at:  
[www.national.com](http://www.national.com)

Products		Design Support	
Amplifiers	<a href="http://www.national.com/amplifiers">www.national.com/amplifiers</a>	WEBENCH® Tools	<a href="http://www.national.com/webench">www.national.com/webench</a>
Audio	<a href="http://www.national.com/audio">www.national.com/audio</a>	App Notes	<a href="http://www.national.com/appnotes">www.national.com/appnotes</a>
Clock and Timing	<a href="http://www.national.com/timing">www.national.com/timing</a>	Reference Designs	<a href="http://www.national.com/refdesigns">www.national.com/refdesigns</a>
Data Converters	<a href="http://www.national.com/adac">www.national.com/adac</a>	Samples	<a href="http://www.national.com/samples">www.national.com/samples</a>
Interface	<a href="http://www.national.com/interface">www.national.com/interface</a>	Eval Boards	<a href="http://www.national.com/evalboards">www.national.com/evalboards</a>
LVDS	<a href="http://www.national.com/lvds">www.national.com/lvds</a>	Packaging	<a href="http://www.national.com/packaging">www.national.com/packaging</a>
Power Management	<a href="http://www.national.com/power">www.national.com/power</a>	Green Compliance	<a href="http://www.national.com/quality/green">www.national.com/quality/green</a>
Switching Regulators	<a href="http://www.national.com/switchers">www.national.com/switchers</a>	Distributors	<a href="http://www.national.com/contacts">www.national.com/contacts</a>
LDOs	<a href="http://www.national.com/ldo">www.national.com/ldo</a>	Quality and Reliability	<a href="http://www.national.com/quality">www.national.com/quality</a>
LED Lighting	<a href="http://www.national.com/led">www.national.com/led</a>	Feedback/Support	<a href="http://www.national.com/feedback">www.national.com/feedback</a>
Voltage References	<a href="http://www.national.com/vref">www.national.com/vref</a>	Design Made Easy	<a href="http://www.national.com/easy">www.national.com/easy</a>
PowerWise® Solutions	<a href="http://www.national.com/powerwise">www.national.com/powerwise</a>	Applications & Markets	<a href="http://www.national.com/solutions">www.national.com/solutions</a>
Serial Digital Interface (SDI)	<a href="http://www.national.com/sdi">www.national.com/sdi</a>	Mil/Aero	<a href="http://www.national.com/milaero">www.national.com/milaero</a>
Temperature Sensors	<a href="http://www.national.com/tempsensors">www.national.com/tempsensors</a>	SolarMagic™	<a href="http://www.national.com/solarmagic">www.national.com/solarmagic</a>
PLL/VCO	<a href="http://www.national.com/wireless">www.national.com/wireless</a>	PowerWise® Design University	<a href="http://www.national.com/training">www.national.com/training</a>

THE CONTENTS OF THIS DOCUMENT ARE PROVIDED IN CONNECTION WITH NATIONAL SEMICONDUCTOR CORPORATION ("NATIONAL") PRODUCTS. NATIONAL MAKES NO REPRESENTATIONS OR WARRANTIES WITH RESPECT TO THE ACCURACY OR COMPLETENESS OF THE CONTENTS OF THIS PUBLICATION AND RESERVES THE RIGHT TO MAKE CHANGES TO SPECIFICATIONS AND PRODUCT DESCRIPTIONS AT ANY TIME WITHOUT NOTICE. NO LICENSE, WHETHER EXPRESS, IMPLIED, ARISING BY ESTOPPEL OR OTHERWISE, TO ANY INTELLECTUAL PROPERTY RIGHTS IS GRANTED BY THIS DOCUMENT.

TESTING AND OTHER QUALITY CONTROLS ARE USED TO THE EXTENT NATIONAL DEEMS NECESSARY TO SUPPORT NATIONAL'S PRODUCT WARRANTY. EXCEPT WHERE MANDATED BY GOVERNMENT REQUIREMENTS, TESTING OF ALL PARAMETERS OF EACH PRODUCT IS NOT NECESSARILY PERFORMED. NATIONAL ASSUMES NO LIABILITY FOR APPLICATIONS ASSISTANCE OR BUYER PRODUCT DESIGN. BUYERS ARE RESPONSIBLE FOR THEIR PRODUCTS AND APPLICATIONS USING NATIONAL COMPONENTS. PRIOR TO USING OR DISTRIBUTING ANY PRODUCTS THAT INCLUDE NATIONAL COMPONENTS, BUYERS SHOULD PROVIDE ADEQUATE DESIGN, TESTING AND OPERATING SAFEGUARDS.

EXCEPT AS PROVIDED IN NATIONAL'S TERMS AND CONDITIONS OF SALE FOR SUCH PRODUCTS, NATIONAL ASSUMES NO LIABILITY WHATSOEVER, AND NATIONAL DISCLAIMS ANY EXPRESS OR IMPLIED WARRANTY RELATING TO THE SALE AND/OR USE OF NATIONAL PRODUCTS INCLUDING LIABILITY OR WARRANTIES RELATING TO FITNESS FOR A PARTICULAR PURPOSE, MERCHANTABILITY, OR INFRINGEMENT OF ANY PATENT, COPYRIGHT OR OTHER INTELLECTUAL PROPERTY RIGHT.

### LIFE SUPPORT POLICY

**NATIONAL'S PRODUCTS ARE NOT AUTHORIZED FOR USE AS CRITICAL COMPONENTS IN LIFE SUPPORT DEVICES OR SYSTEMS WITHOUT THE EXPRESS PRIOR WRITTEN APPROVAL OF THE CHIEF EXECUTIVE OFFICER AND GENERAL COUNSEL OF NATIONAL SEMICONDUCTOR CORPORATION.** As used herein:

Life support devices or systems are devices which (a) are intended for surgical implant into the body, or (b) support or sustain life and whose failure to perform when properly used in accordance with instructions for use provided in the labeling can be reasonably expected to result in a significant injury to the user. A critical component is any component in a life support device or system whose failure to perform can be reasonably expected to cause the failure of the life support device or system or to affect its safety or effectiveness.

National Semiconductor and the National Semiconductor logo are registered trademarks of National Semiconductor Corporation. All other brand or product names may be trademarks or registered trademarks of their respective holders.

Copyright© 2010 National Semiconductor Corporation

For the most current product information visit us at [www.national.com](http://www.national.com)



**National Semiconductor  
Americas Technical  
Support Center**  
Email: [support@nsc.com](mailto:support@nsc.com)  
Tel: 1-800-272-9959

**National Semiconductor Europe  
Technical Support Center**  
Email: [europe.support@nsc.com](mailto:europe.support@nsc.com)

**National Semiconductor Asia  
Pacific Technical Support Center**  
Email: [ap.support@nsc.com](mailto:ap.support@nsc.com)

**National Semiconductor Japan  
Technical Support Center**  
Email: [jpn.feedback@nsc.com](mailto:jpn.feedback@nsc.com)