

RF Reference Design Library

Gallium Arsenide PHEMT

RF Power Field Effect Transistors

Device Characteristics (From Device Data Sheet)

Designed for WLL/MMDS/BWA or UMTS driver applications with frequencies from 1.8 to 3.6 GHz. Devices are unmatched and are suitable for use in Class AB linear base station applications.


- Typical W-CDMA Performance: -42 dBc ACPR, 3.55 GHz, 12 Volts, $I_{DQ} = 55$ mA, 5 MHz Offset/3.84 MHz BW, 64 DPCH (8.5 dB P/A @ 0.01% Probability)
Output Power — 300 mWatt
Power Gain — 11.5 dB
Efficiency — 25%
- 3 Watts P1dB @ 3.55 GHz
- Excellent Phase Linearity and Group Delay Characteristics
- High Gain, High Efficiency and High Linearity
- N Suffix Indicates Lead-Free Terminations

Reference Design Characteristics

- Typical Single-Channel W-CDMA Performance: -45 dBc ACPR, 2.45 GHz, 12 Volts, $I_{DQ} = 55$ mA, 5 MHz Offset/3.84 MHz BW, 64 DPCH (8.5 dB P/A @ 0.01% Probability)
Output Power — 350 mWatt
Power Gain — 12.5 dB
Efficiency — 26%

MRFG35003NT1
MRFG35003MT1
BWA

BWA
2.4-2.5 GHz

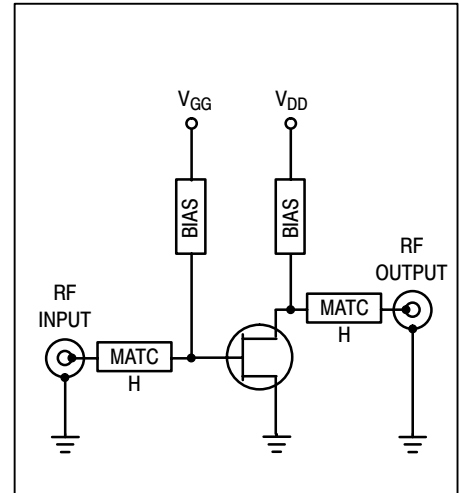

MRFG35003NT1(MT1) BWA 2.4-2.5 GHz REFERENCE DESIGN

Designed by: Monte Miller and Rick Hooper

This reference design is designed to demonstrate the typical RF performance characteristics of the MRFG35003NT1(MT1) when applied for the 2.4-2.5 GHz W-CDMA frequency band. The reference design is tuned for the best tradeoff between good W-CDMA linearity and good power capability and efficiency.

REFERENCE DESIGN LIBRARY TERMS AND CONDITIONS

Freescal Semiconductor is pleased to make this reference design available for your use in development and testing of your own product or products, without charge. The reference design contains easy-to-copy, fully functional amplifier designs. Where possible, it consists of "no tune" distributed element matching circuits designed to be as small as possible, includes temperature compensated bias circuitry, and is designed to be used as "building blocks" for our customers.


HEATSINKING

When operating this fixture please provide adequate heat-sinking for the device. Excessive heating of the device will prevent repeating of the included measurements.

NONLINEAR SIMULATION

To aid the design process and help reduce time to market for our customers, Freescal Semiconductor provides device models for several commercially available harmonic balance simulators. Our model Library is available for all major computer platforms supported by these simulators. For details on the RF model library and supported harmonic balance simulators, go to the following url:

<http://www.freescal.com/rf/models>

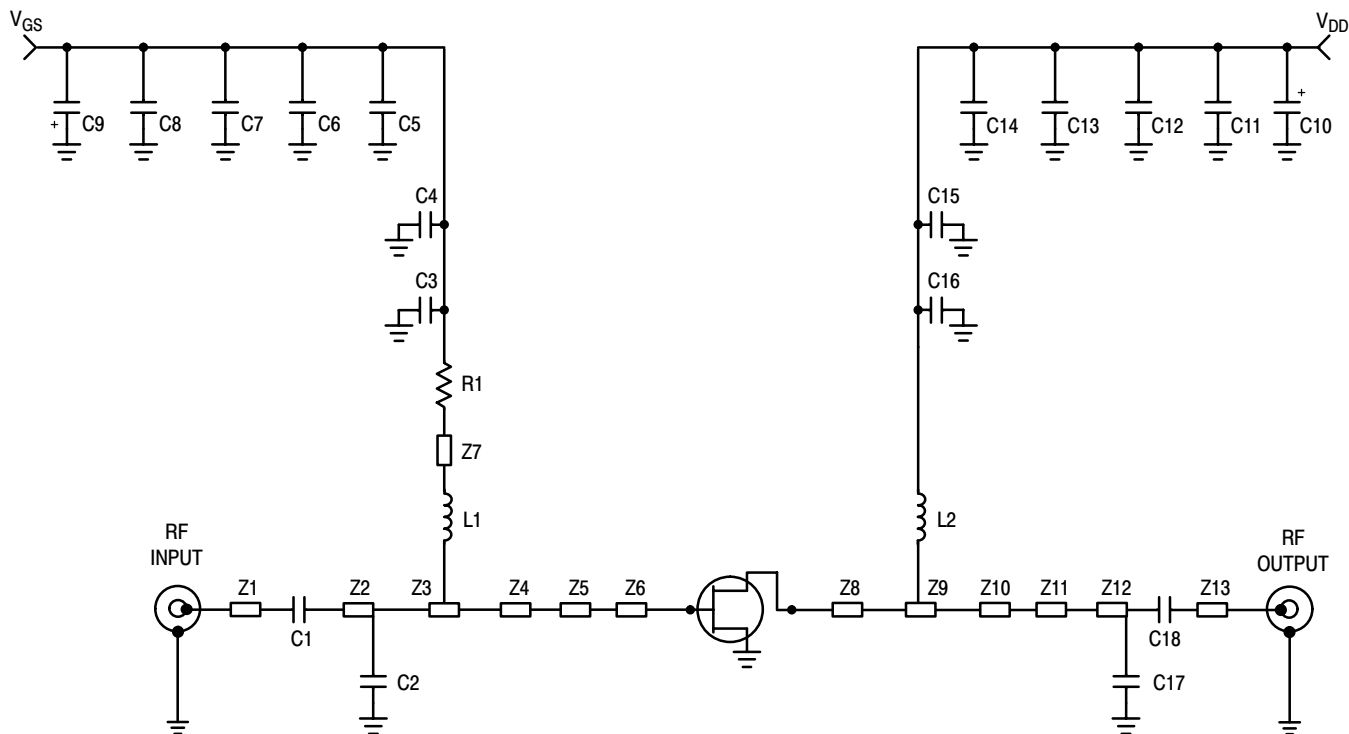


Z1, Z13	0.044" x 0.295" Microstrip	Z7	0.045" x 0.100" Microstrip
Z2	0.044" x 0.730" Microstrip	Z9	0.200" x 0.040" Microstrip
Z3	0.105" x 0.045" Microstrip	Z10	0.260" x 0.020" Microstrip
Z4	0.044" x 0.015" Microstrip	Z11	0.200" x 0.516" Microstrip
Z5	0.340" x 0.320" Microstrip	Z12	0.044" x 0.534" Microstrip
Z6, Z8	0.146" x 0.070" Microstrip	PCB	Rogers 4350, 0.020", $\epsilon_r = 3.50$

Figure 1. MRFG35003NT1(MT1) BWA Reference Design Schematic

Table 1. MRFG35003NT1(MT1) BWA Reference Design Component Designations and Values

Part	Description	Value, P/N or DWG	Manufacturer
C1	3.9 pF Chip Capacitor	08051J3R9BBT	AVX
C2	0.9 pF Chip Capacitor	08051J0R9BBT	AVX
C3, C16	10 pF Chip Capacitors	100A100JP150X	ATC
C4, C15	100 pF Chip Capacitors	100A101JP150X	ATC
C5, C14	100 pF Chip Capacitors	100B101JP500X	ATC
C6, C13	1000 pF Chip Capacitors	100B102JP500X	ATC
C7, C12	0.1 μ F Chip Capacitors	CDR33BX104AKWS	Kemet
C8, C11	39K pF Chip Capacitors	200B393KP500X	ATC
C9, C10	22 μ F Tantalum Capacitors	T491X226K035AS	Newark
C17	1.0 pF Chip Capacitor	08051J1R0BBT	AVX
C18	15.0 pF Chip Capacitor	08051J15R0GBT	AVX
L1	4.7 nH Chip Inductor	LL2102-F4N7K	TOKO
L2	8.2 nH Chip Inductor	LL1608-FHN2K	TOKO
R1	75 Ω , 1/4 W 1% Chip Resistor	D55342M07B75JOR	Newark

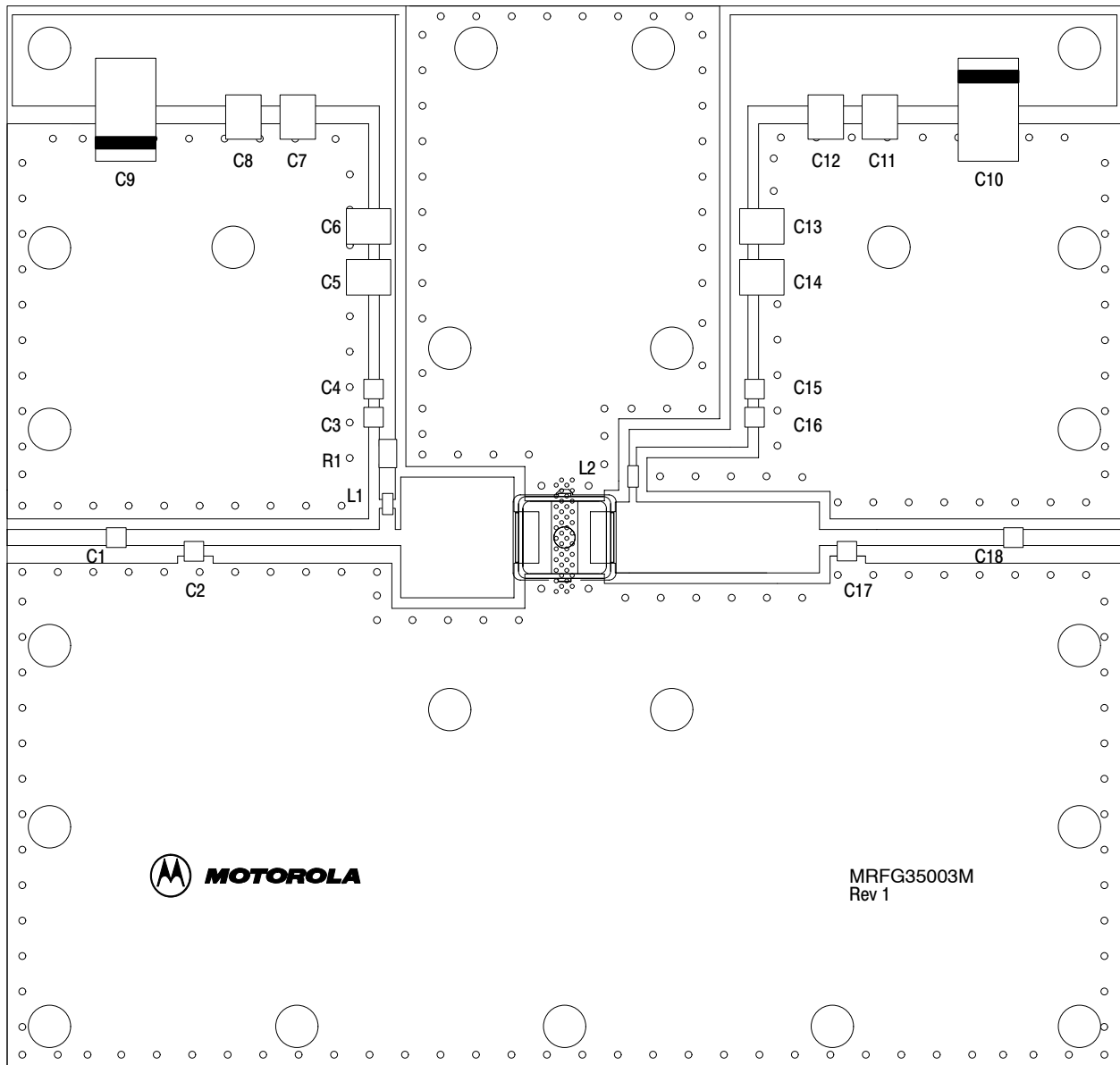

Freescall has begun the transition of marking Printed Circuit Boards (PCBs) with the Freescall Semiconductor signature/logo. PCBs may have either Motorola or Freescall markings during the transition period. These changes will have no impact on form, fit or function of the current product.

Figure 2. MRFG35003NT1(MT1) BWA Reference Design Component Layout

CHARACTERISTICS

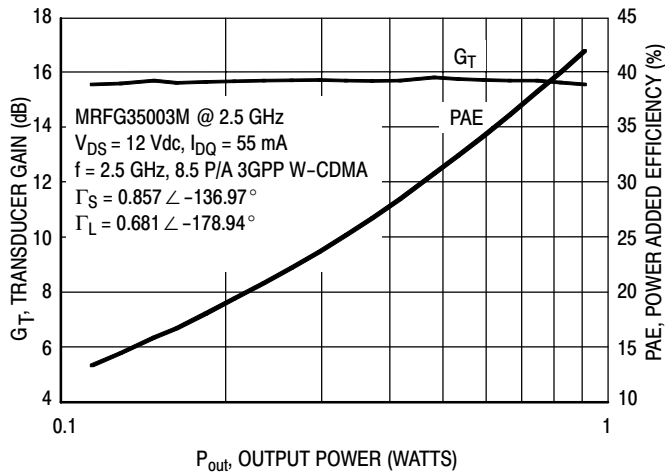


Figure 3. Transducer Gain and Power Added Efficiency versus Output Power

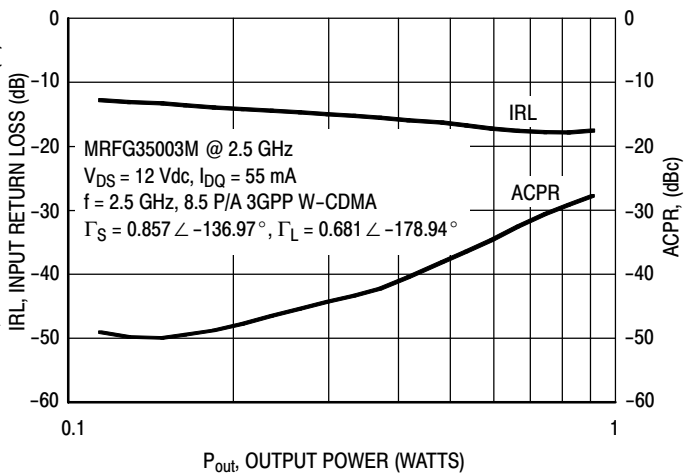


Figure 4. W-CDMA ACPR and Input Return Loss versus Output Power

NOTE: Data in Figures 3 and 4 is generated from load pull, not from the test circuit shown.

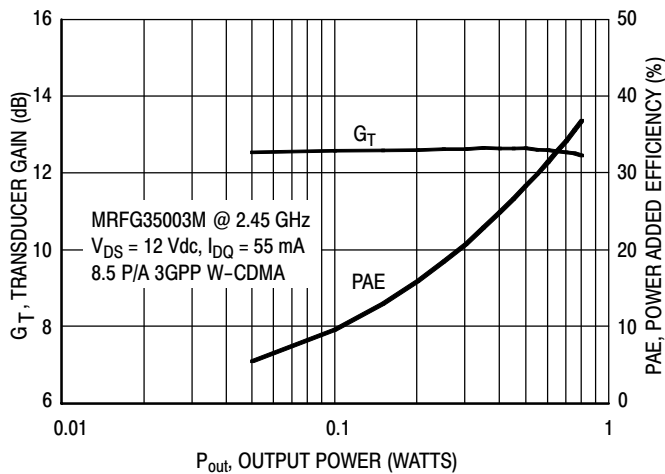


Figure 5. Transducer Gain and Power Added Efficiency versus Output Power

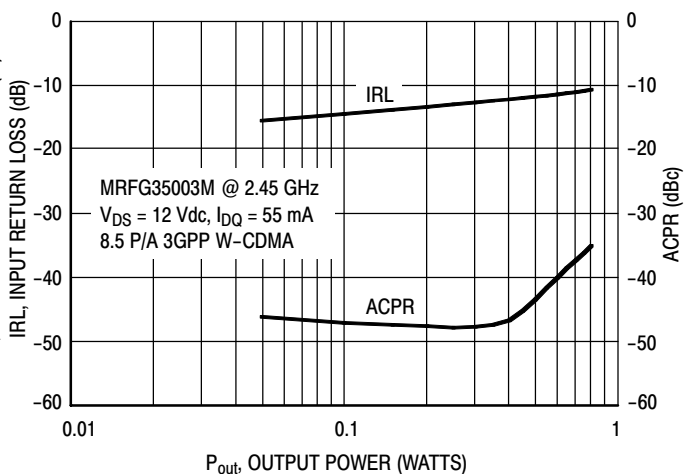


Figure 6. W-CDMA ACPR and Input Return Loss versus Output Power

NOTE: Data in Figures 5 and 6 is generated from the test circuit shown.

How to Reach Us:

Home Page:

www.freescale.com

E-mail:

support@freescale.com

USA/Europe or Locations Not Listed:

Freescale Semiconductor
Technical Information Center, CH370
1300 N. Alma School Road
Chandler, Arizona 85224
+1-800-521-6274 or +1-480-768-2130
support@freescale.com

Europe, Middle East, and Africa:

Freescale Halbleiter Deutschland GmbH
Technical Information Center
Schatzbogen 7
81829 Muenchen, Germany
+44 1296 380 456 (English)
+46 8 52200080 (English)
+49 89 92103 559 (German)
+33 1 69 35 48 48 (French)
support@freescale.com

Japan:

Freescale Semiconductor Japan Ltd.
Headquarters
ARCO Tower 15F
1-8-1, Shimo-Meguro, Meguro-ku,
Tokyo 153-0064
Japan
0120 191014 or +81 3 5437 9125
support.japan@freescale.com

Asia/Pacific:

Freescale Semiconductor Hong Kong Ltd.
Technical Information Center
2 Dai King Street
Tai Po Industrial Estate
Tai Po, N.T., Hong Kong
+800 2666 8080
support.asia@freescale.com

For Literature Requests Only:

Freescale Semiconductor Literature Distribution Center
P.O. Box 5405
Denver, Colorado 80217
1-800-441-2447 or 303-675-2140
Fax: 303-675-2150
LDCForFreescaleSemiconductor@hibbertgroup.com

Information in this document is provided solely to enable system and software implementers to use Freescale Semiconductor products. There are no express or implied copyright licenses granted hereunder to design or fabricate any integrated circuits or integrated circuits based on the information in this document.

Freescale Semiconductor reserves the right to make changes without further notice to any products herein. Freescale Semiconductor makes no warranty, representation or guarantee regarding the suitability of its products for any particular purpose, nor does Freescale Semiconductor assume any liability arising out of the application or use of any product or circuit, and specifically disclaims any and all liability, including without limitation consequential or incidental damages. "Typical" parameters that may be provided in Freescale Semiconductor data sheets and/or specifications can and do vary in different applications and actual performance may vary over time. All operating parameters, including "Typicals", must be validated for each customer application by customer's technical experts. Freescale Semiconductor does not convey any license under its patent rights nor the rights of others. Freescale Semiconductor products are not designed, intended, or authorized for use as components in systems intended for surgical implant into the body, or other applications intended to support or sustain life, or for any other application in which the failure of the Freescale Semiconductor product could create a situation where personal injury or death may occur. Should Buyer purchase or use Freescale Semiconductor products for any such unintended or unauthorized application, Buyer shall indemnify and hold Freescale Semiconductor and its officers, employees, subsidiaries, affiliates, and distributors harmless against all claims, costs, damages, and expenses, and reasonable attorney fees arising out of, directly or indirectly, any claim of personal injury or death associated with such unintended or unauthorized use, even if such claim alleges that Freescale Semiconductor was negligent regarding the design or manufacture of the part.

Freescale™ and the Freescale logo are trademarks of Freescale Semiconductor, Inc. All other product or service names are the property of their respective owners.
© Freescale Semiconductor, Inc. 2005. All rights reserved.

