
The TUA 6100 direct down conversion tuner IC in BICMOS technology combines bipolar analog functions with a CMOS-PLL on one chip. This integration reduces external discrete components (SAW filter) and provides the potential to reduce the cost. Our TSSOP-28 package saves PCB-board space. The tuner IC is suitable for multimedia applications like DVB/DSS systems (set-top boxes, PC card receiver) and new applications, such as digital SAT TV sets and digital VCRs.

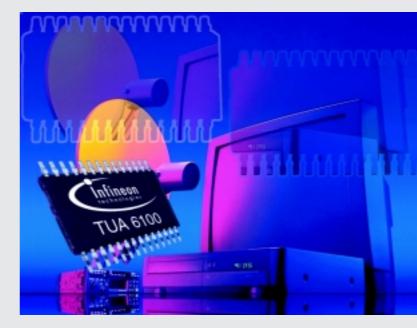Next generation DCR IC in development - goes for higher integration and smaller package (VQFN).



## **Potential Application**

- Digital set-top box (DVB, DSS)
- VCR digital (satellite-ready)
- TV (satellite-ready)
- PC card receiver

### **Features**

- Low impendance gain controlled RF input
- Dual matched double balanced mixer
- Digital generation of 0°/90° LO signal
- Direct down conversion from1. IF (LNB output) to baseband
- IF filter not necessary
- I/O for external basebandfilter
- CMOS PLL-Synthesizer
- Active loopfilter
- 3 high current switch outputs
- Low noise reference voltage
- 3-wire-Bus/I<sup>2</sup>C-Bus
- P-TSSOP-28 package
- Buffered Xtal output

## **Price projection**

- Standard price list
- For Key and Focus accounts or high volumes you may contact your regional Infineon sales partner

# **Development and Support Tools**

- NIM Module for Satellite Frontend
- Evaluation Board TUA 6100
- PLL Programming Kit for Windows (16 Bit)

Features	Benefits
Direct down conversion from 1. IF to	Fully integrated single-chip frontend
baseband	
CMOS PLL-Synthesizer	On board low phase noise PLL
	solution
IF filter not necessary	Lower BOM-SAW filter eliminated
3-wire-Bus / I <sup>2</sup> C-Bus	Two bus systems available
P-TSSOP-28 package	Small package - space saving

### **Packing**


Туре	Ordering Code	Package	Availability
TUA 6100	Q67037-A1034P	P-TSSOP-28	MP Q3/2000 for key accounts ES Q2/2000
Infineon NIM Module	Q6703-A1151		Q3/2000
Infineon/STM NIM Module	Q6703-A1152		Q3/2000

MP = Mass Production ES = Engineering Sample
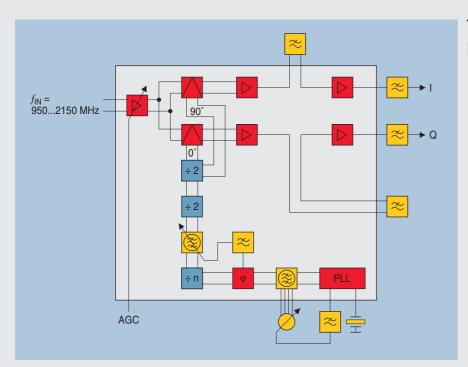
# TUA 6100

Direct Conversion Tuner IC for Digital Satellite Receiption






# TUA 6100 Block Diagram

Documentation	Date of Issue/Version
Specification	05/00
Application/Measurement	05/00
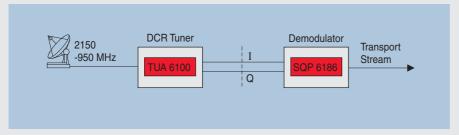
# Infineon Strength

Complete DCR solution with fitting feature size

- TUA 6100: PLL on chip
- SQP 6186: DISEqC 2.x, SCPC/ MCPC range 1...45 MSymb/s,
- analog filtering on board, integrated AGC + equalizer
- Cost savings due to unnecessary external filtering
- Interface to other demodulator tested - NIM module available



# TUA 6100 Application Example

How to reach us: http://www.infineon.com

Published by Infineon Technologies AG, Bereich Kommunikation, St.-Martin-Strasse 53, D-81541 München

© Infineon Technologies AG 2000. All Rights Reserved.

### Attention please

The information herein is given to describe certain components and shall not be considered as warranted characteristics.

Terms of delivery and rights to technical change reserved.

We hereby disclaim any and all warranties, including but not limited to warranties of non-infringement, regarding circuits, descriptions and charts stated herein.

Infineon Technologies is an approved CECC manufacturer.

### Information

For further information on technology, delivery terms and conditions and prices please contact your nearest Infineon Technologies Office in Germany or our Infineon Technologies Representatives worldwide.

### Varnings

Due to technical requirements components may contain dangerous substances. For information on the types in question please contact your nearest Infineon Technologies Office.

Infineon Technologies Components may only be used in lifesupport devices or systems with the express written approval of Infineon Technologies, if a failure of such components can reasonably be expected to cause the failure of that life-support device or system, or to affect the safety or effectiveness of that device or system. Life support devices or systems are intended to be implanted in the human body, or to support and/or maintain and sustain and/or protect human life. If they fail, it is reasonable to assume that the health of the user or other persons may be endangered.